



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

OCC OF DC SHUNT GENERATOR

Expt. No:

Date:

Objective:

To obtain the open circuit characteristics of the given DC shunt generator at its rated speed and determine the Critical resistance and Critical speed.

Apparatus:

S.No	Name of the Equipment	Range	Number


Name plate details:

Fuse ratings:



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Circuit Diagram:

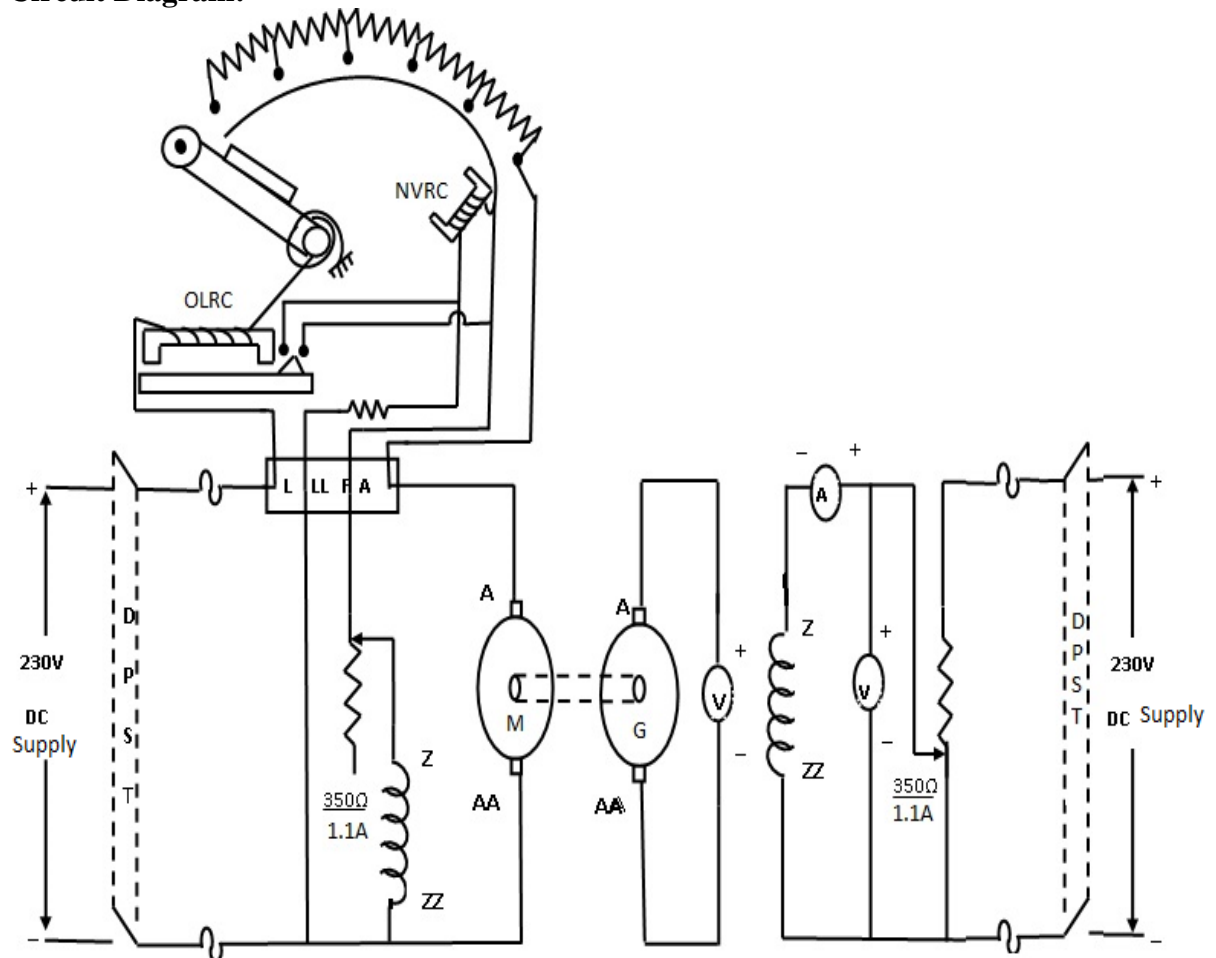

Theory:

The O.C.C is a curve showing the relationship between the no load emf generated and the shunt field current (E_o and I_f). Even when the field current is zero there is some residual magnetism present in the poles. Hence there is a small voltage generated even at zero field current, which is called the residual voltage. As the field current is increased, E_o also increases and the curve traced is almost a straight line. As I_f is further increased the poles start getting saturated, the straight line relation no longer holds good and the curve bends and becomes almost horizontal.

In a D.C. generator, for any given speed, the induced emf in the armature is directly proportional to the flux per pole.

$$E_g = (\Phi Z N P) / 60 A \text{ Volts}$$

Where Φ is the flux per pole in webers,

Z is the no. of conductors in the armature,

N is the speed of the shaft in rpm,

P is the no. of poles and

A is the no. of parallel paths.



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

A = 2 (wave)

A = P (lap)

Critical resistance:

It is that value of resistance in the field circuit at which the generator will just excite (or voltage build up begins). If the resistance is higher, the machine will fail to build up voltage. It is given by the slope of the tangent drawn to the linear portion of the magnetization curve from the origin.

Conditions for voltage build up in a d.c shunt generator

1. There should be some residual magnetism in the poles.
2. For the given direction of rotation, the shunt field coils should be properly connected.
3. The coils should be so connected that the flux generated by the field current aids the residual flux.
4. When excited at no load, the shunt field circuit resistance should be less than the critical resistance.

Critical speed:

It is that value of speed at which the given shunt field resistance represents the critical resistance.


Procedure:

1. Connections are made as per the circuit diagram.
2. Motor field rheostat is kept in minimum position.
3. Generator field rheostat is kept in maximum position.
4. D.C. Generator is driven at its rated speed with the help of prime mover (DC shunt motor).
5. Gradually the field rheostat of generator is varied in steps to get field current in steps and armature terminal voltage is measured in each step.
6. Step 5 is repeated till 120% of rated voltage is obtained.
7. Then, the field current of generator is decreased and the armature terminal voltage is noted in each step.
8. The O.C.C curve is plotted



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

GRAPHS:

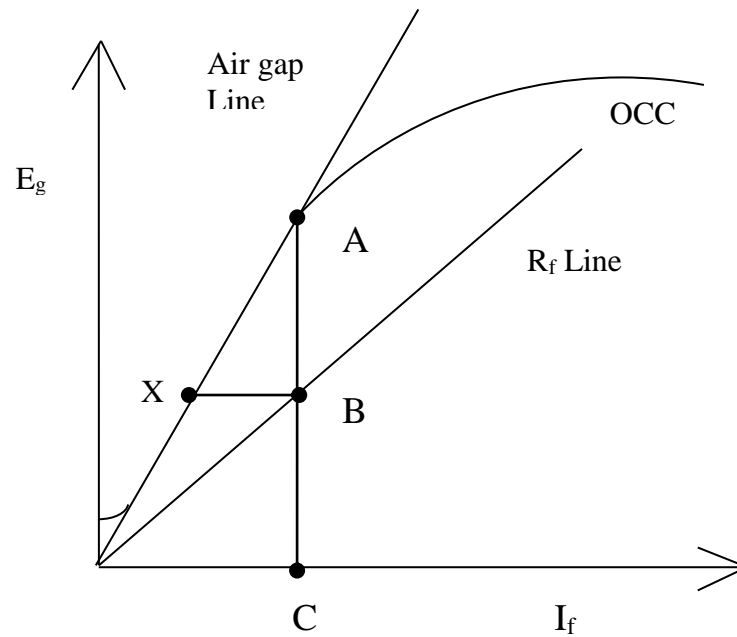

Critical Speed $N_c = (BC/AC) * N_s$

Critical Resistance = AB/BX

RESULT:

REMARKS IF ANY:



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Viva Questions:

1. What is residual voltage? How is it measured?
2. What is critical resistance? How can it be determined?
3. What are the conditions necessary for voltage build up in a d.c shunt generator?
4. What is critical speed?
5. Mention the characteristics of dc generators?



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

BRAKE TEST ON DC COMPOUND MOTOR

Expt. No:

Date:

Objective:

To conduct brake test on DC compound motor for long shunt cumulative & differential connections and to draw the performance characteristics.

Apparatus:

S.No	Name of the Equipment	Range	Number

Name plate details:


Fuse ratings:



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Circuit Diagram:


Cumulative Compound Motor:

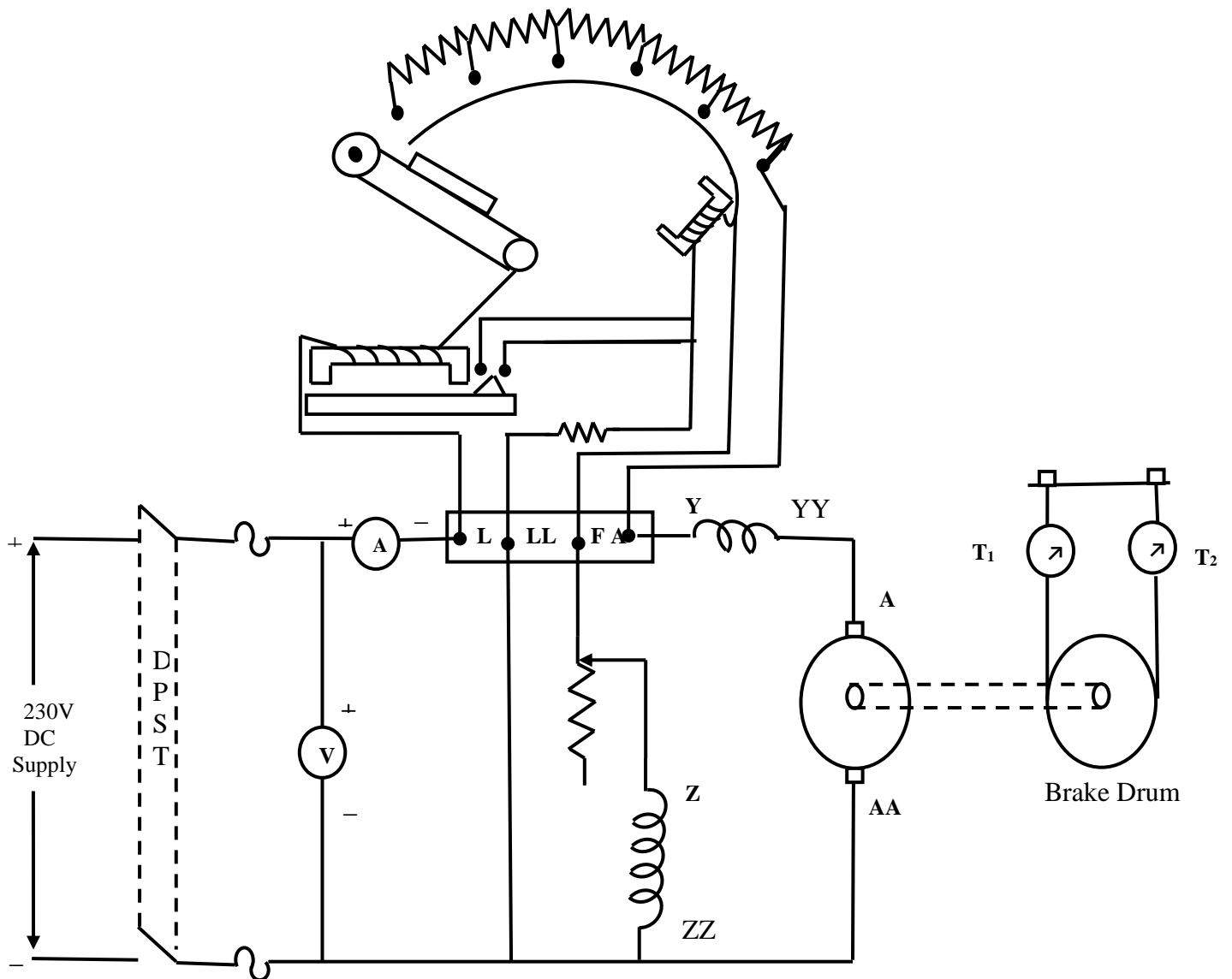



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Differential Compound Motor:

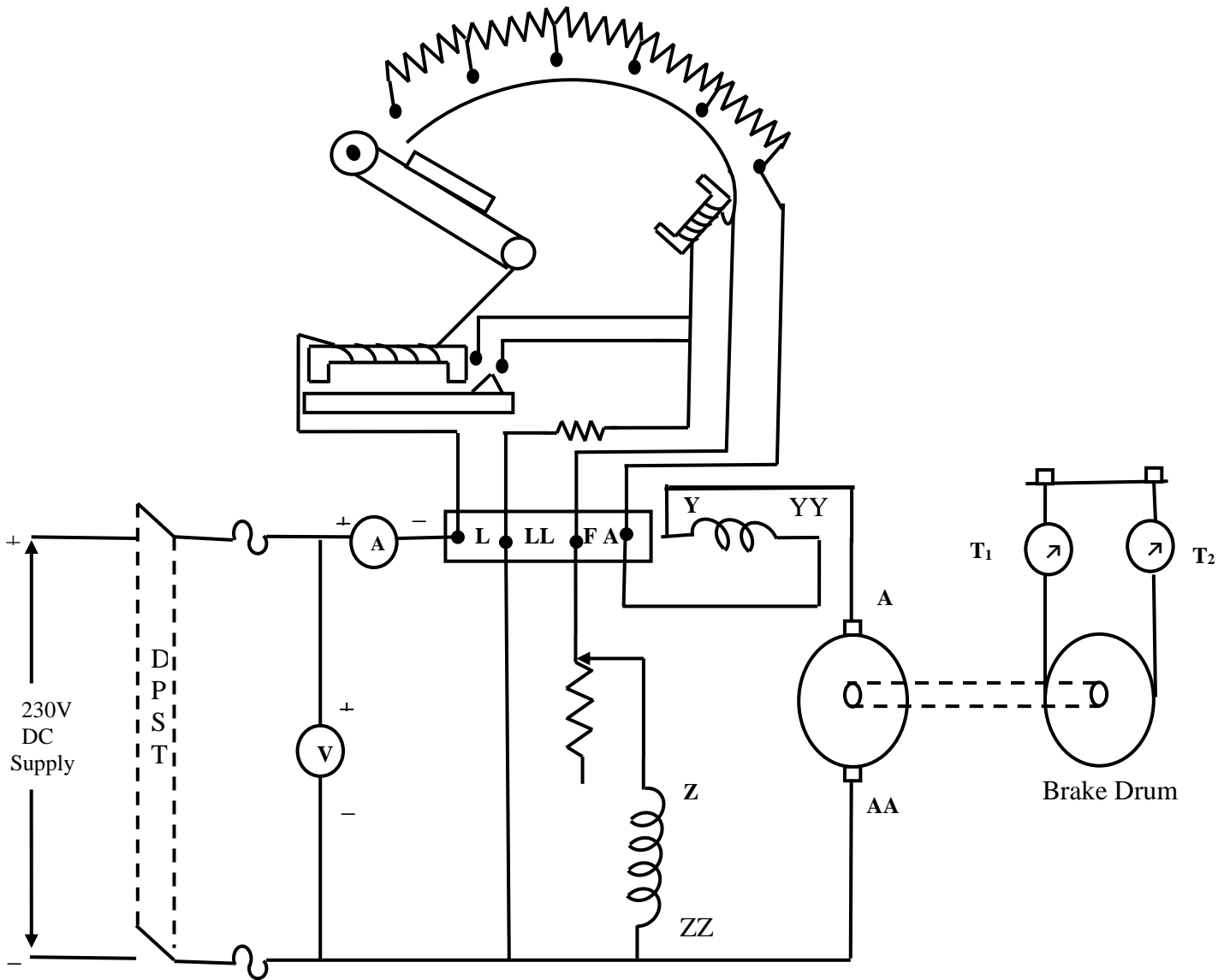



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Theory:

This is a direct method of testing a dc compound motor as a cumulative and as a Differential compound motor. In this method, a rope is wound round the pulley and its two ends attached to two spring balances S_1 and S_2 . The tensions on the rope T_1 and T_2 can be adjusted with the help of swivels. The force acting tangentially on the pulley is equal to the difference between the readings of the two spring balances. Power developed in the motor at the shaft = $P_{out} = T \times \omega$ watts

where $\omega = (2\pi N) / 60$ (N is speed in r.p.m)

$$T_{shaft} = F \times r \text{ Newton-meter} = (T_1 - T_2) \text{ Kg} * 9.8 * r$$

$$\text{Motor output } P_{out} = T_{shaft} \times \omega = (2\pi N T_{shaft}) / 60$$

(R is radius of the pulley in meter and 1kg wt = 9.8 Newton)

Total power input to the motor $P_{in} =$ Power input to the field

$$P_{in} = V I_L$$

$$\% \text{ Efficiency} = (P_{out} / P_{in}) * 100$$

In a separately excited cumulatively compound motor Φ_{sh} is constant. Hence, Φ_{se} increases with increase in the load or armature current. Thus, the speed drops at a faster rate in a cumulative compound motor than in a shunt motor.

$$T_a = K \Phi I_a.$$

Where $\Phi = \Phi_{sh} + \Phi_{se}$; Φ_{sh} is constant. Φ_{se} increases with increase in I_a . Hence T_a increases.

If Φ_{sh} is stronger than Φ_{se} , the $T_a \sim I_a$ characteristic and Speed ~Torque characteristic approaches to the shunt motor characteristics. If Φ_{se} is stronger than Φ_{sh} , above characteristics approaches to the series motor characteristics.

In a Differential Compound motor, the series flux opposes the shunt flux. With increase in I_a , the net flux in the air gap decreases. Thus, the motor speed increases slightly with load.

Hence, it can be designed to give a constant speed under all load conditions.

Procedure:

- 1) Circuit is connected as per the circuit diagram.
- 2) The field rheostat of motor is kept at minimum position.
- 3) Machine is started at no load initially, speed is adjusted with the help of its rheostat at the rated speed and meter readings are noted.
- 4) By increasing load on the brake drum and by tightening the belt the corresponding meter readings are noted.
- 5) The same procedure is followed for differential compound motor also.



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Differential Compound Motor:

Voltage(V)	I _L (A)	Speed (N) (RPM)	Balance		Torque T=(T ₁ ~T ₂)rg (Nm)	O/p= $\frac{2\pi NT}{60}$	I/p= V I _L	%η= [O/p / I/p]*100
			T ₁ Kg	T ₂ Kg				

Sample Calculations:

Cumulative compounding:

Input Voltage (V)= 224 V

Input current = I_L= 4.8 A

N= 1602 rpm

T₁ = 0.3 kg; T₂ =2.7 kg.

T=(T₁-T₂)rg = (2.7-0.3)80.155*9.8 = 3.64 Nm

Output = O/p= $\frac{2\pi NT}{60}$ = $\frac{2*3.14*1602*3.64}{60}$ = 610.65 W

Input = VI_L= 224*4.8 = 1075.2W

%Efficiency = %η=[(O/p) / (I/p)]*100 = 610.65/1075.2 = 56.2%



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Differential Compounding:

Input Voltage (V)= 225 V

Input current = $I_L = 3.2$ A

$N = 1670$ rpm

$T_1 = 0.2$ kg; $T_2 = 0.9$ kg.



$T = (T_1 - T_2)rg = (0.9 - 0.2) * 0.155 * 9.8 = 1.06$ Nm

Output = $O/p = (2\pi NT)/60 = (2 * 3.14 * 1670 * 1.06)/60 = 185.67$ W

Input = $V I_L = 225 * 3.2 = 720$ W

%Efficiency = $\% \eta = [(O/p) / (I/p)] * 100 = 185.67/720 = 25.7\%$

Graphs:

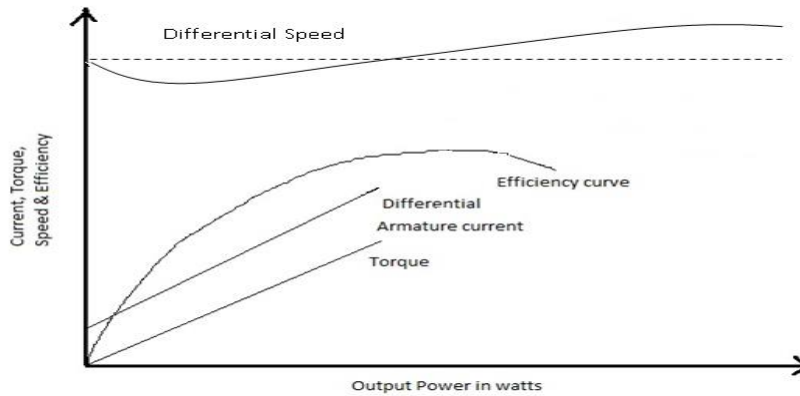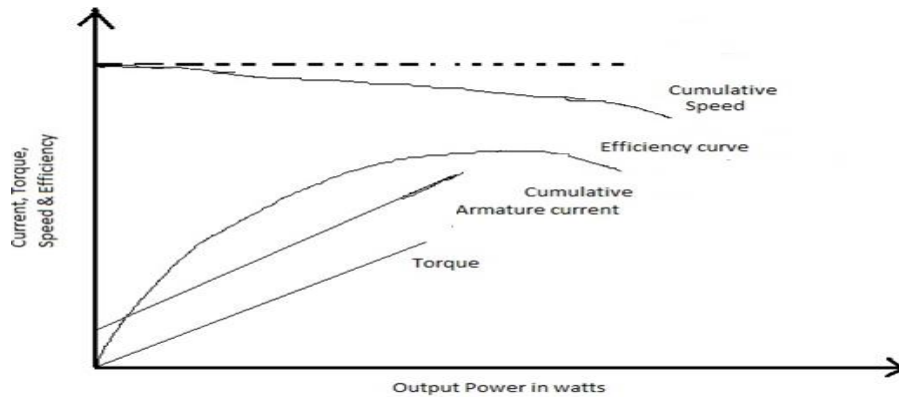

Result:

Remarks if any:



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Viva Questions:

1. On what principle does DC motor operates?
2. What are the applications of DC Compound motors?
3. What is the typical brush drop in DC motors?
4. Draw different characteristic curves of DC compound motors?
5. Write the difference between cumulative compound and differentially compound dc motor?



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

SWINBURNE'S TEST

Expt. No:

Date:

Objective:

To conduct Swinburne's test on DC shunt machine and to predetermine its efficiency both as a Generator and Motor.

Apparatus:

S.No	Name of the Equipment	Range	Number


Name plate details:

Fuse rating:



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Circuit Diagram:

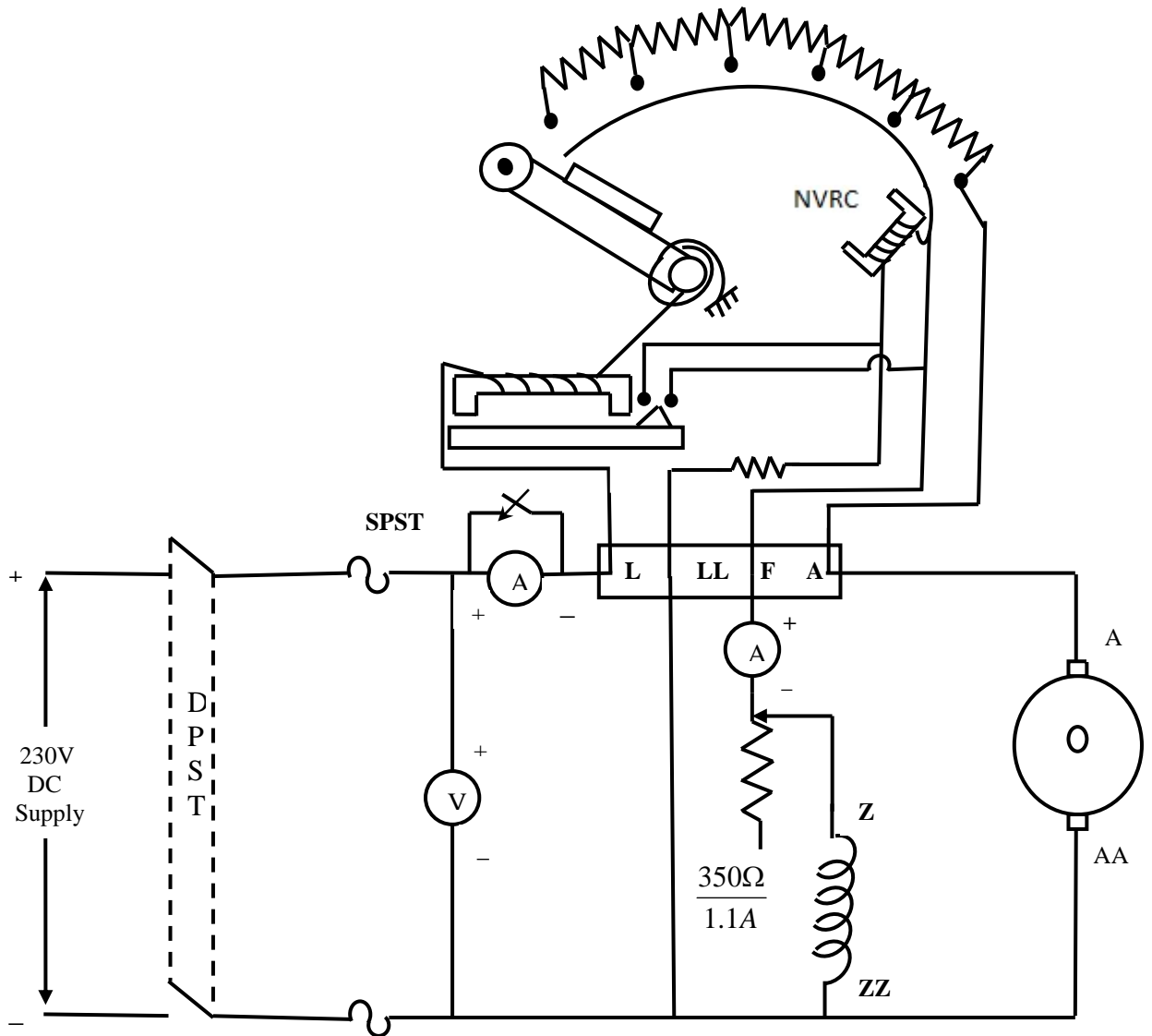



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Theory:

Testing of D.C. machines can be divided into three methods: (a) direct, (b) regenerative, and (c) indirect Swinburne's Test is an indirect method of testing a D.C. machine. In this method, the constant losses of the D.C. machine are calculated at no-load. Hence, its efficiency either as a motor or as a generator can be pre-determined. In this method, the power requirement is very small. Hence, this method can be used to pre-determine the efficiency of higher capacity D.C. machines as a motor and as a generator.

Disadvantages:

- (1) Efficiency at actual load is not accurately known.
- (2) Temperature rise on load is not known.
- (3) Sparking at commutator on load is not known.

Losses in a D.C. Machine:

The losses in a D.C. machine can be divided as 1) Constant losses, 2) Variable losses, which changes with the load.

Constant losses:

Mechanical Losses: Friction and Windage losses are called mechanical losses. They depend upon the speed. A D.C. shunt machine is basically a constant speed machine both as a generator and as a motor. Thus, the mechanical losses are constant.

Iron Losses: For a D.C. shunt machine, the field current hence the flux. Hence, hysteresis and eddy current losses (which are also called as iron losses) remain constant.

Field Copper Losses: Under normal operating conditions of a D.C. shunt machine, the field current remains constant. Thus, power received by the field circuit (which is consumed as field copper losses) is constant. Constant losses in a D.C. shunt machine = Mechanical losses + Iron Losses + Field copper losses

Variable Losses:

The power lost in the armature circuit of a D.C. machine increases with the increase in load. Thus, the armature copper losses are called as variable losses.

Procedure:

1. Connections are made as per the circuit diagram.
2. Motor field rheostat is kept in minimum position.
3. The SPST switch is kept in closed position on no load.
4. Supply is given & motor is started with the help of four-point starter.
5. The field rheostat is adjusted till the rated speed is achieved.
6. Switch is opened and currents I_L , I_F & Voltmeter reading are noted.
7. The efficiency of machine is calculated both as motor and generator by assuming the load to be increased in steps from no-load to rated value.



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Formulae used:

$$\text{No Load armature current} = I_{a0} = 2.02A$$

$$\text{No Load input} = VI_{L0} \text{ Watts} = 220 * 2.8 = 616W$$

$$\text{No Load armature Cu loss} = I_{a0}^2 R_a = 2.02^2 * 3.5 = 44.88W$$

$$\text{Shunt field loss} = VI_f = 220 * 0.78 = 171.6W$$

$$\text{Constant losses of machine, } P_c = VI_{L0} - I_{a0}^2 R_a - VI_f = 616 - 44.88 - 171.6 = 399.52W$$

$$\text{Where } I_a = \text{Armature current (at any load)} \quad R_a = \text{Armature resistance} = 3.5\Omega$$

As Motor:

$$\text{Load current} = I_L \text{ amps} = 6A$$

$$\text{Field current} = I_f \text{ amps} = 0.78A$$

$$\text{Armature cu loss} = I_a^2 R_a \text{ watts} = (5.722)^2 * 3.5 = 114.59W$$

$$I_a = I_L - I_f = 6 - 0.78 = 5.22A$$

$$\text{Total losses, } P_L = P_c + \text{armature 'cu' loss} + \text{Shunt field losses} = 399.52 + 114.59 + 171.6 = 685.71W$$

$$\text{Input power} = V I_L \text{ watts} = 220 * 6 = 1320W$$

$$\text{Output power} = \text{input} - \text{total losses} = VI_L - P_L \text{ Watts} = 1320 - 685.71 = 634.29W$$

$$\text{Efficiency} = (\text{output}/\text{input}) * 100 = (VI_L - P_L / VI_L) * 100 = (634.29/1320) * 100 = 48.05\%$$

As Generator:

$$\text{Load current} = I_L \text{ amps} = 6A$$

$$\text{Field current} = I_f \text{ amps} = 0.78A$$

$$I_a = I_L + I_f = 6.78A$$

$$\text{Armature cu loss} = I_a^2 R_a \text{ watts} = (6.78)^2 * 3.5 = 160.88W$$

$$\text{Total losses, } P_L = P_c + \text{Armature 'cu' loss} + \text{Shunt field losses} = 399.52 + 160.88 + 171.6 = 732W$$

$$\text{Output power} = V I_L \text{ watts} = 220 * 6 = 1320W$$


$$\text{Input power} = \text{Output} + \text{total losses} = VI_L + P_L = 1320 + 732 = 2052Watts$$

$$\text{Efficiency} = (\text{output}/\text{input}) * 100 = (VI_L / VI_L + P_L) * 100 = (1320/2052) * 100 = 64.32\%$$



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Graphs:

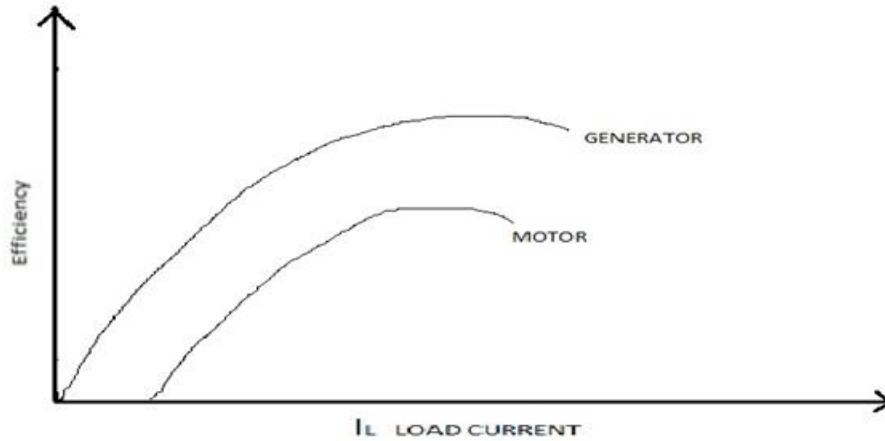

Result:

Remarks if any:



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Viva Questions:

1. What is the purpose of Swinburne's test?
2. What are constant losses in a DC machine?
3. What are the assumptions made in Swinburne's test?
4. Why is the indirect method preferred over direct loading test?
5. The efficiency of DC machine is generally higher when it is working as a generator than when is working as a motor. Is this statement true or false?
Justify your answer with proper reasons



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

SPEED CONTROL OF DC SHUNT MOTOR

Expt. No:

Date:

Objective:

To conduct an experiment on DC shunt motor for its speed control using
(i) Flux control method (ii) Armature control method.

Apparatus:

S.No	Name of the Equipment	Range	Number


Name plate details:

Fuse ratings:



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Circuit diagram:

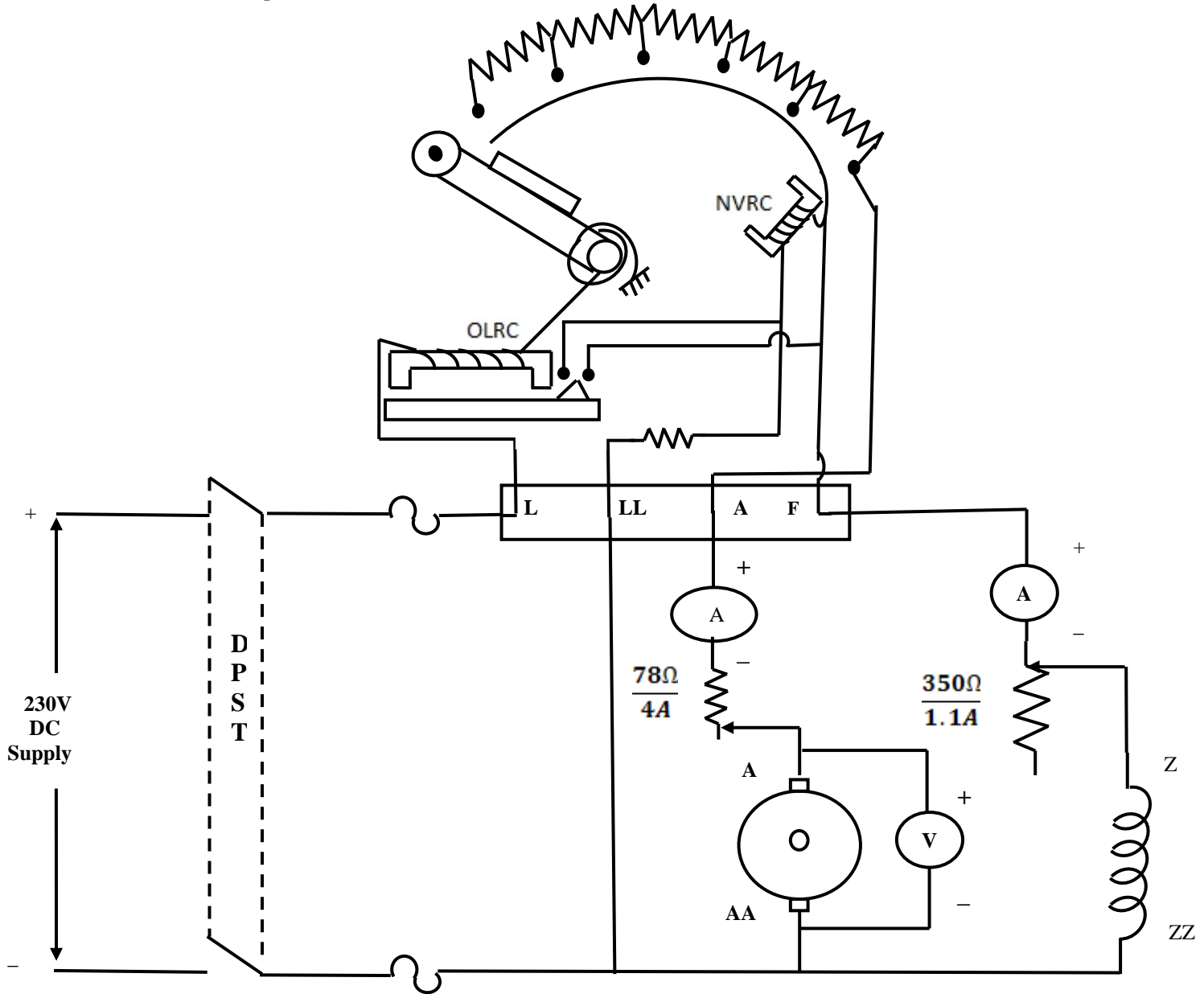



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Theory:

Any D.C. motor can be made to have smooth and effective control of speed over a wide range. The shunt motor runs at a speed defined by the expressions.

$$E_b = \Phi ZNP/60A \text{ and } E_b = V - I_a R_a$$

$$N = (V - I_a R_a) / K\Phi \text{ where } K = ZP/60A$$

Since $I_a R_a$ drop is negligible $N \propto 1/\Phi$ or $N \propto 1/I_f$

Where N is the speed, V is applied voltage, I_a is the armature current, and R_a is the armature resistance and Φ is the field flux.

Speed control methods of shunt motor:

1. Applied voltage control.
2. Armature rheostat control.
3. Field flux control.

Applied voltage control:

In the past, Ward-Leonard method is used for Voltage control method. At present, variable voltage is achieved by SCR controlled AC to DC converter unit is used to control the speed of a motor. In this method, speed control is possible from rated speed to low speeds.

Armature rheostat control:

Speed control is achieved by adding an external resistance in the armature circuit. This method is used where a fixed voltage is available. In this method, a high current rating rheostat is required.

Disadvantages:

- (a) Large amount of power is lost as heat in the rheostat. Hence, the efficiency is low.
- (b) Speed above the rated speed is not possible. The motor can be run from its rated speed to low speeds.

Field flux control:

Speed control by adjusting the air gap flux is achieved by means of adjusting the field current i.e., by adding an external resistance in the field circuit. The disadvantage of this method is that at low field flux, the armature current will be high for the same load. This method is used to run the motor above its rated speed only.

Procedure:



Armature Control Method:

1. Connections are made as per the circuit diagram.
2. Motor field rheostat is kept in minimum position.
3. Armature rheostat is kept in maximum position.
4. The DC supply is switched on and the motor is started with the help of starter.
5. The speed of the motor is measured with the help of the tachometer and the voltage across the armature and the field current is noted.
6. The speed is changed by varying the rheostat in the armature circuit. During this period, the field current is constant.
7. The voltage across the armature, the field current and the speed are noted down.



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Graphs:

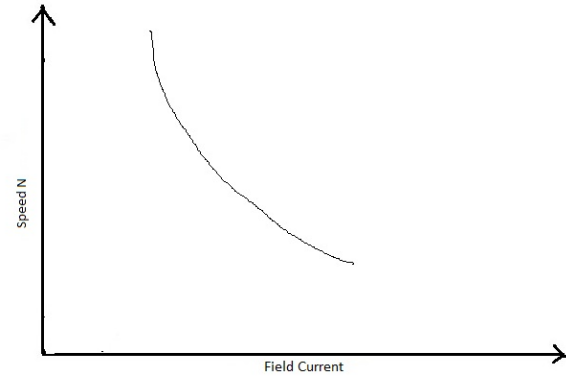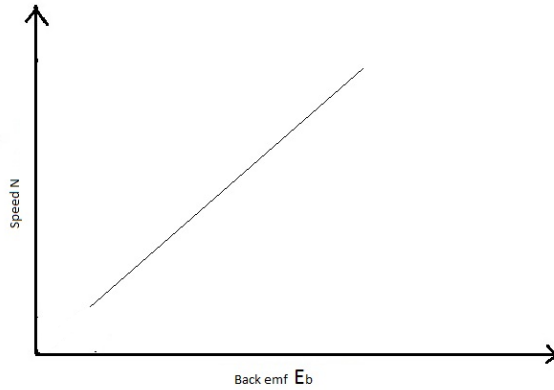

Result:

Remarks if any:



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Viva Questions:

1. How does the speed of a DC shunt motor vary with armature voltage and field current?
2. Compare the resistance of the armature and field winding.
3. What is the importance of speed control of DC motor in industrial applications?
4. Which is of the two methods of speed control is better and why?
5. Why is the speed of DC shunt motor practically constant under normal load condition?



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

HOPKINSON'S TEST

Expt. No:

Date:

Objective:

To conduct Hopkinson's test on two identical DC machines and determine their efficiencies.

Apparatus:


S.No	Name of the Equipment	Range	Number

Name plate details:



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Circuit Diagram:

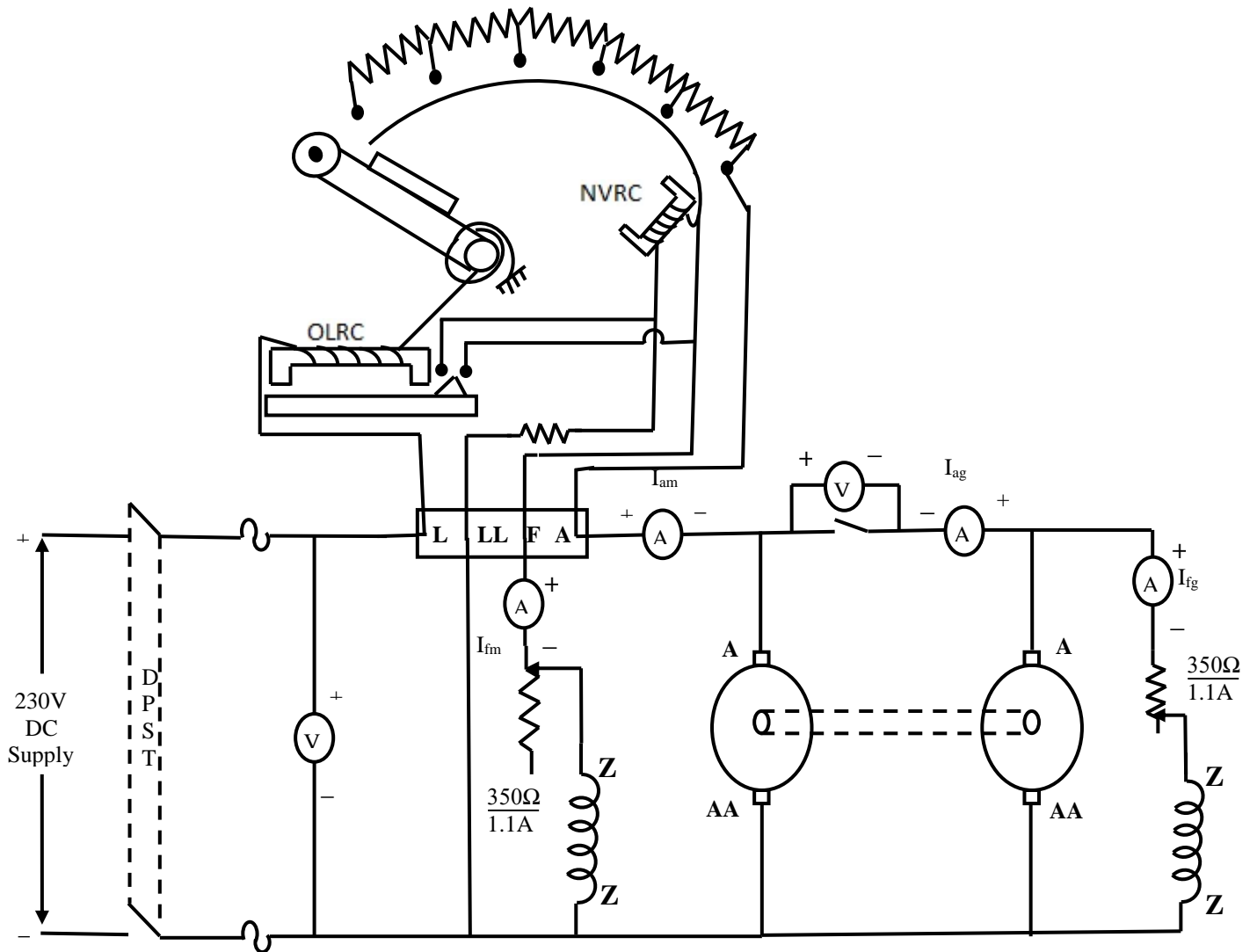



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Theory:

To find efficiency of a dc shunt machine, the best method is to directly load it and measure its output and input. For large rating machines the direct load test method is difficult to conduct due to a) It is costly to obtain a suitable load and b) The amount of energy to be spent for testing is too large. For, these reasons, electrical engineers use indirect methods like Swinburne's test, Separation of losses, and the Retardation test etc, are used to determine the efficiency. These tests are simple to carry out but they offer no information about how the machine performs under actual load conditions. Also, because of assumptions the results obtained are not so accurate.

Hopkinson's test (also called Regenerative or Back-to-Back test) offers the advantages of load test without its disadvantages. By this method, full-load test can be carried out on two identical shunt machines without wasting their outputs. The two machines are mechanically coupled and are so adjusted that one of them runs as a motor and the other as a generator. The mechanical output of the motor drives the generator. The generator emf value is brought to the bus bar voltage and then paralleled it to bus bars. The electrical output of the generator is used in supplying the greater part of input to the motor. If there were no losses in the machines, then they would have run without any external power supply. But due to losses, generator output is not sufficient to drive the motor and vice versa. Thus, these losses in the machines are supplied electrically from the supply mains.

Procedure:

1. Circuit is connected as shown in the circuit diagram.
2. The motor field rheostat is kept at minimum position and generator field rheostat is kept at maximum position.
3. Motor is started with the help of starter at no load.
4. The motor is to be made to run at rated speed by adjusting the motor field rheostat value.
5. The generator field resistance is varied so that voltmeter reads zero volts across the SPST switch, at that moment SPST switch is closed.
6. The generator field resistance is varied in steps and corresponding readings are noted.



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Sample Calculations:

Calculation of Efficiencies:

I_{am} = Current drawn by the motor from the mains = 3.5A

I_{ag} = Current supplied by the generator to the motor = 2A

I_{fm} = Field current of motor = 0.7A

I_{fg} = Field current of generator = 0.64A

V = Supply voltage = 220V

The electrical output of the generator plus the small power taken from the supply, equal to the power drawn by the motor as a mechanical power after supplying the motor losses.

Motor input = $V(I_{am} + I_{ag} + I_{fm}) = 220(3.5 + 2 + 0.7) = 1364W$

Generator output = $VI_{ag} = 220 * 2 = 440W$

R_a = armature resistance of each machine

Armature copper losses in a generator = $(I_{ag} + I_{fg})^2 * R_{ag} = (2 + 0.64)^2 * 2.04 = 14.21W$

Armature copper losses in a motor = $(I_{am} + I_{ag})^2 * R_{am} = (3.5 + 2)^2 * 2.09 = 63.22W$

Shunt copper losses in a generator = $V * I_{fg} = 220 * 0.64 = 140.8W$

Shunt copper losses in a motor = $V * I_{fm} = 220 * 0.7 = 154W$

Motor and Generator losses are equal to the power supplies by the mains.

Power drawn from supply = $VI_{am} = 220 * 3.5 = 770W$

Stray losses of both the machines = $W_{TS} = VI_{am} - [(I_{am} + I_{ag})^2 * R_{am} + (I_{ag} + I_{fg})^2 * R_{ag} + (I_{fg})^2 * R_{shg}] = 770 - (63.22 + 14.21 + 140.8) = 692.7W$ Watts

Therefore, total stray losses for the set $W_{Ts} = 692.7$ Watts

The stray losses are approximately equal in two machines.

Stray losses per machine = $W_s = W_{TS} / 2 = 346.35W$

For Generator:

Total losses $W_g = (I_{ag} + I_{fg})^2 * R_{ag} + I_{fg} V + W_s = 14.21 + 140.8 + 346.35 = 501.26W$

Output = $VI_{ag} = 220 * 2 = 440W$

Therefore % efficiency $(\eta_g) = (VI_{ag} / (VI_{ag} + W_g)) * 100 = [440 / (440 + 501.26)] * 100 = 46.74\%$

For Motor:

Total losses = $W_m = (I_{am} + I_{ag})^2 * R_{am} + V * I_{fm} + W_s = 63.22 + 154 + 346.35 = 563.57W$




G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

$$\text{Input } P_{in} = V(I_{am} + I_{ag} + I_{fm}) = 1364 \text{ W}$$

$$\text{Output } P_o = P_{in} - W_m = 1364 - 563.57 = 800.47 \text{ W}$$

$$\text{Therefore \% efficiency } (\eta_m) = (P_o / P_{in}) * 100 = (800.47 / 1364) * 100 = 58.69\%$$

Graphs:

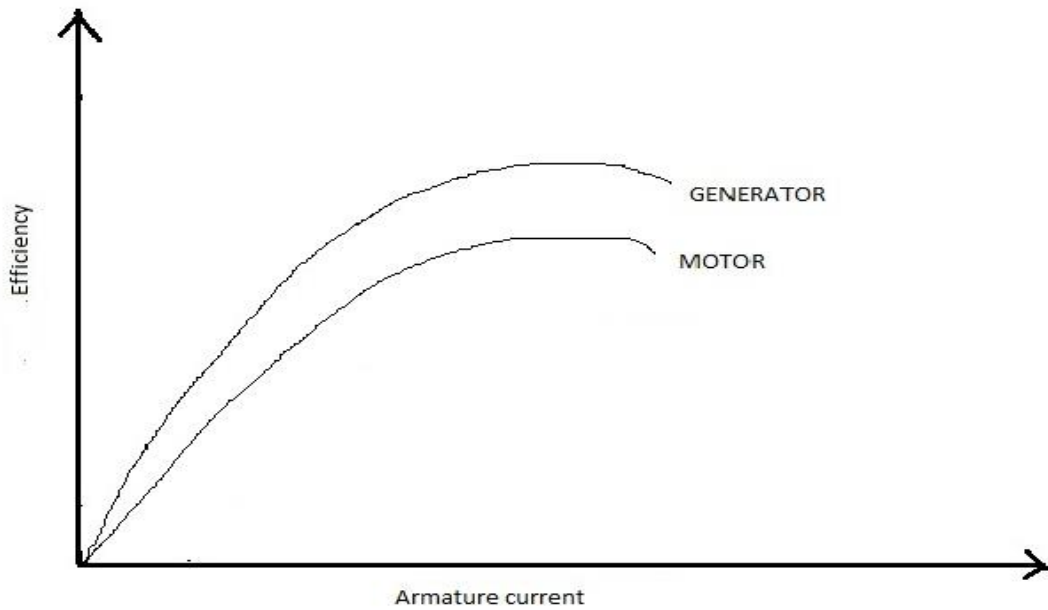

Result:

Remarks if any:



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Viva Questions:

1. What is the need of conducting Hopkinson's test?
2. Why this test is known as regenerative test?
3. What is the purpose of voltmeter connected across the SPST switch?
4. The efficiency is more for dc machine when working as a generator than when working as a motor operation. Explain why?
5. What is the significance of back emf in DC motors?



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

FIELD'S TEST ON TWO IDENTICAL DC SERIES MACHINES

Expt. No:

Date:

Objective:

To conduct Field's test on two identical DC series machines and to calculate the efficiency of a given DC series machine.

Apparatus:


S.No	Name of the Equipment	Range	Number

Name plate details:



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Circuit Diagram:

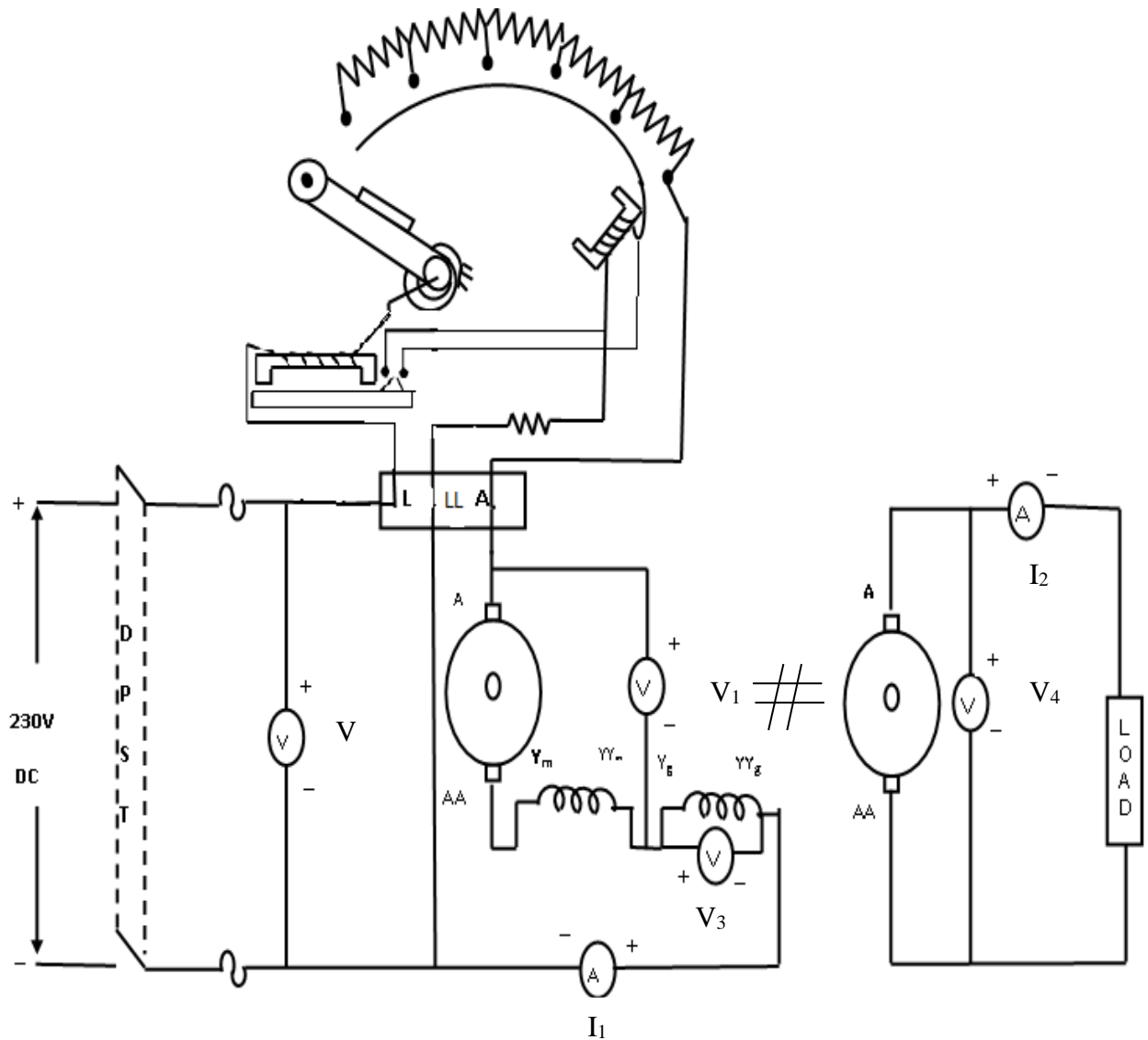

Theory:

In a series motor, the field winding is connected in series with the armature winding. Thus the same current flows through the field and armature windings.

Electrical characteristics(T vs I_a) :-

It shows the variation of torque with the armature current. We have $T \propto \Phi I_a$ where Φ is the flux/pole $\propto I_a$ (as $\Phi \propto I_a$ up to the point of magnetic saturation)

Thus $T \propto I_a^2$

However after magnetic saturation Φ remains almost constant, Hence $T \propto I_a$. Thus the curve is a parabola up to magnetic saturation and shows a linear variation after the point.



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Mechanical Characteristics: (N vs T):- It shows the variation of speed with torque.

We have $N \propto E_b / \Phi$ as E_b is almost constant where E_b is back emf

In a series motor $\Phi \propto I_a$ and therefore $N \propto 1 / I_a$

That is, as I_a increases, Speed decreases.

The same pattern is followed in the N-T characteristics. The curve traced is a rectangular hyperbola.

A series motor should never be started at no load. At no load, I_a is very small, hence the speed of the motor becomes dangerously high (as $N \propto 1 / I_a$).

Formulae used:

$$\text{Total input} = V I_1$$

$$\text{Total output} = V_4 I_2$$

$$\text{Total Losses} = \text{input} - \text{output}$$

$$\text{Armature copper losses} = (R_{am} + R_{sem} + R_{seg}) I_1^2 + I_2^2 R_{ag}$$

$$\text{Stray losses of each machine} = (\text{Total losses} - \text{Armature copper losses}) / 2$$

$$\text{Motor efficiency} = [V_1 I_1 - I_1^2 (R_a + R_{se}) - \text{Stray losses}] / V_1 I_1$$

$$\text{Generator efficiency} = V_4 I_2 / [V_4 I_2 + I_2^2 R_a + I_1^2 R_{seg} + \text{stray losses}]$$

R_{am} = Motor Armature resistance

R_{sem} = Motor series field winding resistance

R_{seg} = Generator series field winding resistance

R_{ag} = Generator Armature resistance

Procedure:

1. The mechanical coupled machines are connected as shown in the circuit diagram.
2. Before switching on the supply, sufficient load on generator is ensured.
3. Supply is given and the machine set is started gradually using a 3 –point starter.
4. The load is adjusted on generator until rated speed is obtained.
5. Ammeter and voltmeter readings are taken and efficiency is calculated.



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Observations:

V (V)	V ₁ (V)	V ₃ (V)	V ₄ (V)	I ₁ (A)	I ₂ (A)	Speed (rpm)

Sample Calculations:

$$\text{Total input} = V I_1 \text{ Watts} = 200 * 13.6 = 2720W$$

$$\text{Total output} = V_4 I_2 \text{ Watts} = 230 * 7.2 = 1656W$$

$$\text{Total Losses} = \text{input} - \text{output Watts} = 2720 - 1656 = 1064W$$

$$\text{Armature copper losses} = (R_{am} + R_{sem} + R_{seg}) I_1^2 + I_2^2 R_{ag} \text{ Watts} = (1.3 + 0.38 + 1.16) * 13.6^2 + 7.2^2 * 2.17 = 637.77W$$

$$\text{Stray losses of each machine} = (\text{Total losses} - \text{Armature copper losses}) / 2 \text{ Watts} = (1064 - 637.77) / 2 = 213.115W$$

$$\text{Motor efficiency} = ([V_1 I_1 - I_1^2 (R_a + R_{se}) - \text{Stray losses}] / V_1 I_1) * 100 = [(180 * 13.6 - 13.6^2 * 1.68 - 213.115) / 180 * 13.6] * 100 = 78.6$$

$$\text{Generator efficiency} = (V_4 I_2 / [V_4 I_2 + I_2^2 R_a + I_1^2 R_{seg} + \text{stray losses}]) * 100 = 230 * 7.2 / [(230 * 7.2 + 7.2^2 * 2.17 + 213.115 + 13.6 * 1.16)] * 100 = 75.4$$

Result:

Remarks if



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Viva Questions:

1. Why a DC series motor/generator should never be started on no - load?
2. Why a DC series motor has a high starting torque?
3. Compare the resistances of the field windings of DC shunt and series motor?
4. What are the applications of DC series motors and generators?
5. Comment on the Speed – Torque characteristics of a DC series motor.



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

OC, SC TESTS ON 1- Φ TRANSFORMER

Expt. No:

Date:

Objective:

To conduct OC, SC test on a 1- Φ transformer and hence pre-determine its efficiency and % regulation at different loads and also to determine the equivalent circuit parameters.

Apparatus:

S.No	Name of the Equipment	Range	Number

Name plate details:


Fuse ratings:




G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

CIRCUIT DIAGRAM:

OPEN CIRCUIT TEST:

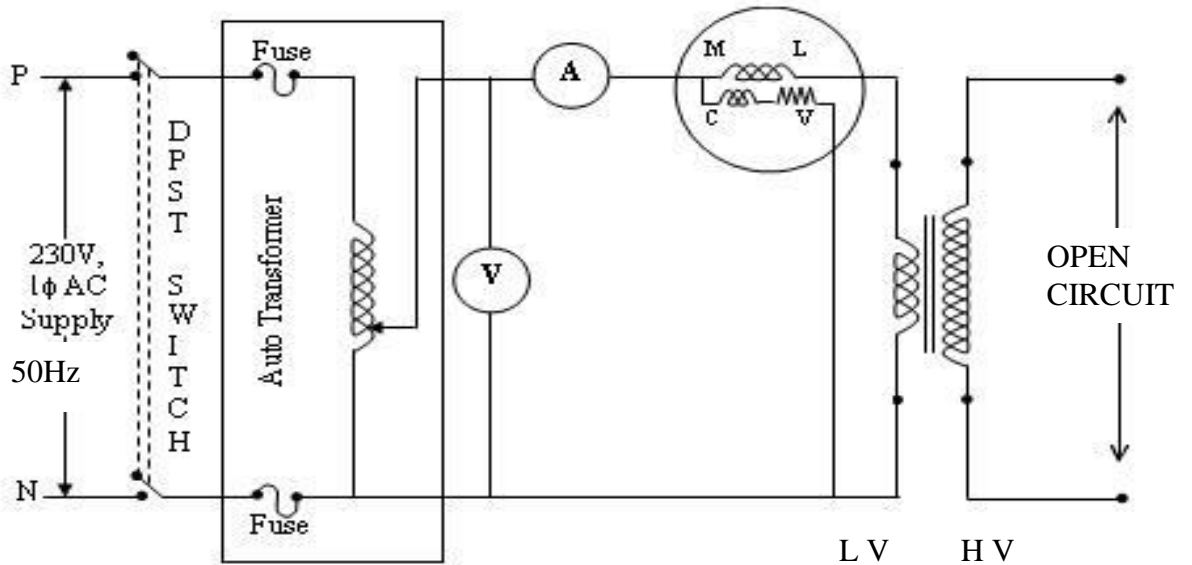

SHORT CIRCUIT TEST:

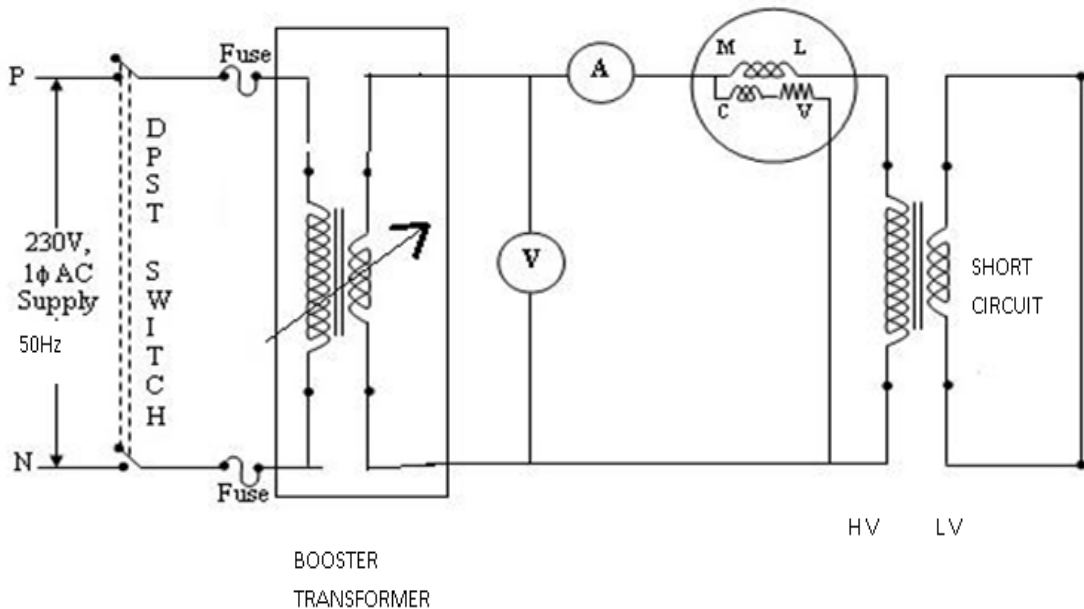



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Theory:

A transformer is a static device which transfers the electrical energy from one circuit to another circuit without any change in the frequency. The transformer works on the principle of electromagnetic induction between two windings placed on a common magnetic circuit. These two windings are electrically insulated from each other and also from the core. The losses in a transformer are (i) magnetic losses or core losses (ii) ohmic losses or copper losses. The losses of a transformer, magnetic losses and ohmic losses can be determined by performing (a) open circuit test and (b) short circuit test. From the above tests, the efficiency and regulation of a given transformer can be predetermined at any given load. The power consumed during these tests is very less as compared to the load test.

Open Circuit Test:

In open circuit test, usually HV side is kept open and meters are connected on LV side as shown in the circuit diagram. When rated voltage is applied to the LV side, the ammeter reads the no-load current I_0 and wattmeter reads the power input. The no load current I_0 is 2 to 5% of full load current. Hence, the copper losses at no-load are negligible. Iron losses are the sum of hysteresis and eddy current losses.

$$W_o = V_{LV} I_0 \cos\phi_0$$

Short Circuit Test:

This test is performed to determine the equivalent resistance and leakage reactance of the transformer and copper losses at full – load condition. In this test usually LV side is shorted and meters are connected on HV side. A variable low voltage is applied to the HV winding with the help of booster transformer. This voltage is varied till the rated current flows in the HV side or LV side. The voltage applied is 5 to 10 percent of rated voltage, while the rated current flows in the windings. The wattmeter indicates the full load copper losses and core losses at V_{SC} . But the iron losses at this low voltage are negligible as compared to the iron losses at the rated voltage.

Procedure:

O.C.TEST:

1. Connect the circuit as per the circuit diagram.
2. Rated voltage is applied to circuit on low voltage side with the help of auto transformer with high voltage side open.
3. All meter readings are taken.



S.C. TEST:

1. Connect the circuit as per the circuit diagram.
2. Rated current is applied to circuit on high voltage side with the help of booster transformer with low voltage side short-circuited.
3. All meter readings are taken.



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

GRAPHS:

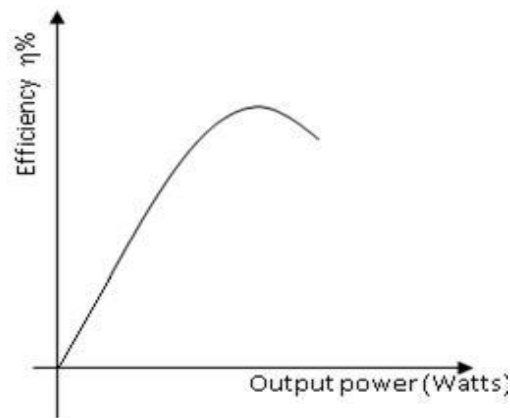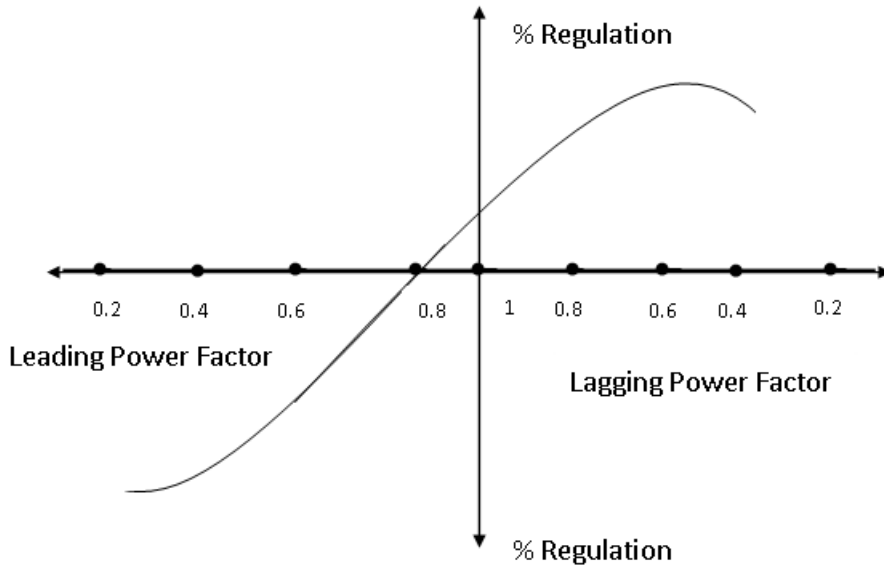

Load (x)



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

SAMPLE CALCULATIONS:

Calculation of R_0 and X_0 of equivalent circuit from O.C test

$$V_0 = 230V, I_0 = 0.4 \text{ A}, W_0 = 38.4 \text{ Watts}$$

$$\text{Iron losses} = W_0 = V_0 I_0 \cos\phi_0$$

$$\cos\phi_0 = W_0 / V_0 I_0 = 38.4 / 230 * 0.42 = 0.417$$

$$\cos\phi_0 = 0.417 \quad \sin\phi_0 = 0.9095$$

$$I_m = I_0 \sin\phi_0 = 0.4 * \sin(65.33) = 0.3635 \text{ A}, I_w = I_0 \cos\phi_0 = 0.4 * 0.417 = 0.167 \text{ A}$$

LV SIDE:

$$R_0 = V_0 / I_w = 230 / 0.167 = 1377.24 \Omega$$

$$X_0 = V_0 / I_m = 230 / 0.3635 = 632.737 \Omega$$

$$K = V_2 / V_1 = 400 / 230 = 1.73$$

$$\text{HV Side: } R_0 = \text{LV side } R_0 \times K^2 = 1377.24 * 1.73^2 = 4121.96 \Omega ; \text{ HV side}$$

$$X_0 = \text{LV side } X_0 \times K^2 = 632.737 * 1.73^2 = 1893.72 \Omega$$

Where K = Turns ratio

SC TEST:

Calculation of R_{01} and X_{01} for equivalent circuit

$$I_{sc} = 5 \text{ A}, V_{sc} = 25.2 \text{ V}, W_{sc} = 120 \text{ Watts}$$

$$\text{Full load copper losses or variable losses} = W_{sc} = I_{sc}^2 R_{02} = 120$$

$$R_{02} = W_{sc} / I_{sc}^2 = 120 / 5^2 = 4.8 \Omega \quad Z_{02} = V_{sc} / I_{sc} = 25.2 / 5 = 5.04 \Omega$$

$$X_{02} = \sqrt{(Z_{02}^2 - R_{02}^2)} = 2.014 \Omega$$

Calculation of percent regulation from SC test (% Voltage Regulation)

$$\text{At full load current, } I_2 = 8.6 \text{ A}, V_2 = 230 \text{ V}, \text{ p.f} = \cos\Phi = 0.8 \text{ lag}$$

$$\text{Percent regulation (\% V.R)} = (I_2 R_{02} \cos\Phi \pm I_2 X_{02} \sin\Phi) / V_2$$

(Note: + for lagging and – for leading power factors)

$$\% \text{ V.R} = [8.6 * 4.8 * 0.8 + 8.6 * 2.014 * 0.6] / 230 = 3.61$$

$$\% \text{ V.R} = [8.6 * 4.8 * 0.8 - 8.6 * 2.014 * 0.6] / 230 = 5.89$$



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))


Efficiency Calculation from O.C and S.C tests

$$\% \eta = \frac{XV_2 I_2 \cos \Phi}{XV_2 I_2 \cos \Phi + \text{Iron losses } (W_0) + \text{Copper losses at load } X (X^2 W_{sc})}$$

At full load 0.8 power factor where $X = \text{load}$ (varies from 0 to 1)

$$\% \eta = \frac{1/4 * 230 * 8.6 * 0.8}{1/4 * 230 * 8.6 * 0.8 + 38.4 + (1/4)^2 * 120} = \frac{395.6}{441.5} = 89.6$$

Diagram of Equivalent circuit of the transformer:

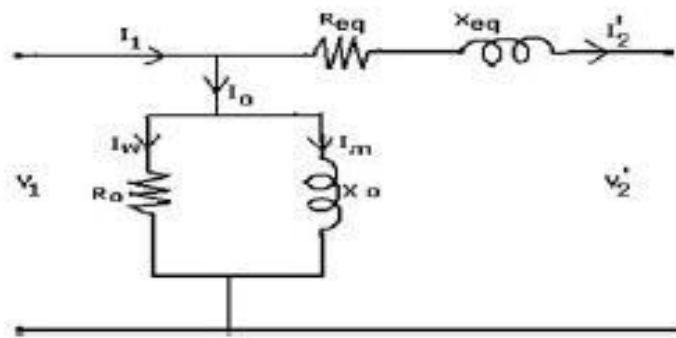

RESULT:

REMARKS IF ANY:



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Viva Questions:

1. In OC test power supply is connected to low voltage side but in SC test power supply is connected to high voltage side of the transformer. Why?
2. How we will find (or) Identify the L.V winding and H.V winding of the transformer just by observing the outer part of the transformer. [Here number of turns are not known]
3. Why R_1 , X_1 and R_0 , X_m in equivalent circuit of transformer are called as linear parameters and non-linear parameters?
4. Why R_1 , X_1 and R_0 , X_m are connected in respective positions? Can't they be interchanged?
5. Why OC test is to be conducted at rated voltage and SC test at rated current? What will happen if tests are conducted at other than those rated voltages.



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

SCOTT CONNECTION OF TRANSFORMERS

Expt. No:

Date:

Objective:

To make Scott connection of transformers and to draw characteristics at balanced and unbalanced loads.

Apparatus:

S.No	Name of the Equipment	Range	Number


Name plate details:

Fuse ratings:



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

CIRCUIT DIAGRAM:

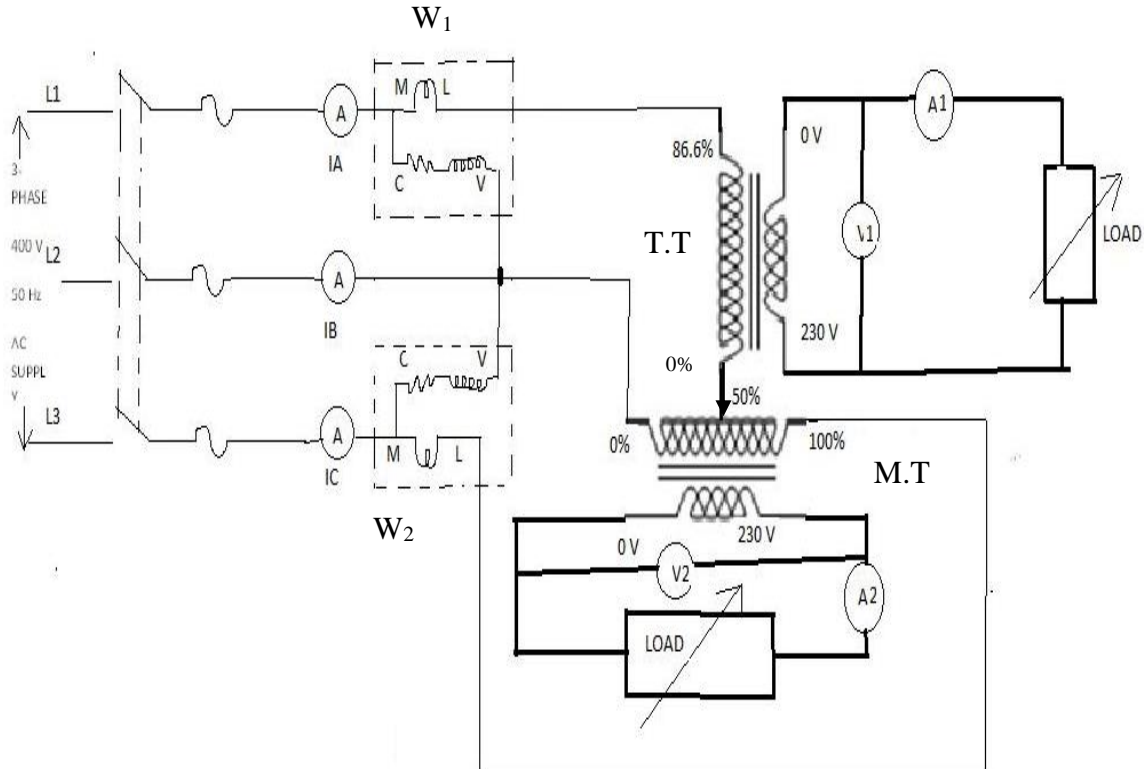

Theory:

Scott connection is one by which 3-phase to 2-phase transformation is accomplished with the help of two identical Transformers having same current rating. One Transformer has a center tap on primary side and it is known as Main transformer. It forms the horizontal member of the connection. Another Transformer has 0.866tap on primary side and known as Teaser transformer. The 50% tap point on primary side of the main Transformer is joined to 86.6% tap on primary of the teaser Transformer. Obviously full rating of the Transformer is not at all used. Refer to the Fig.1. The main Transformer primary winding center tap point D is connected to one end of the primary of the teaser on secondary side, both the main & teaser Transformer turns are used (not only 86.6%). Hence the voltage per turn will be equal for both Transformer. Since point D is located midway on CB, V_{AD} leads V_{CB} by 90° i.e, voltages across primary are 90° . Similarly, the phase angle difference between two secondary voltages V_{ad} & V_{bc} will be 90° which confirms 2- Φ system on the secondary. Position of Neutral point N on primary side: Remember point D is not the neutral on primary, since its voltages w.r.t A, B, C are not equal to $V_L/\sqrt{3}$ i.e, the neutral point is that one which gives equal voltage with A, B, C. The neutral point is one third the way down the teaser transformer winding from A to D or point N divides the teaser primary winding in the ratio of 1:2. Hence the neutral



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

must be at $86.6/3=28.8\%$ from D. The secondaries of the two transformers gives two phase supply with 90° phase difference.

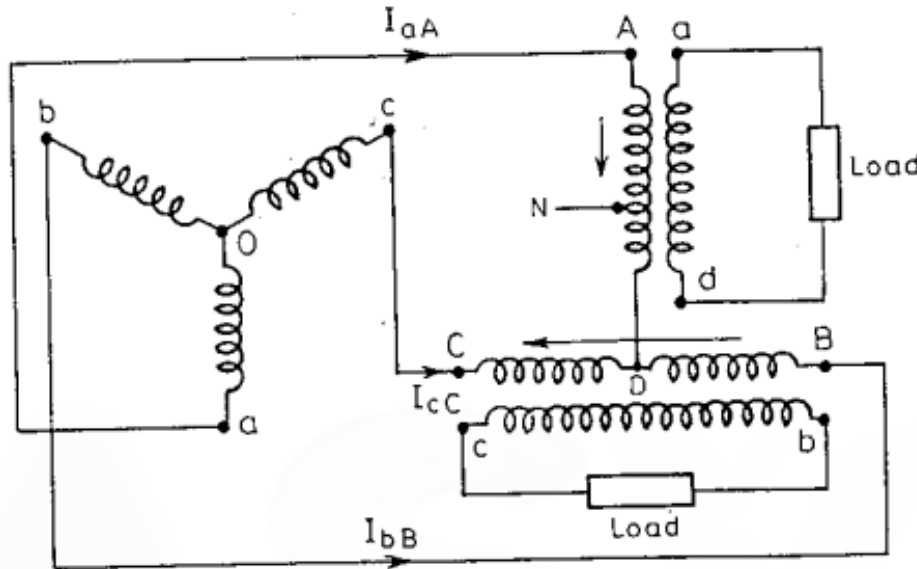


Figure 1 Schematic connection diagram

Procedure:

1. Circuit is connected as per the circuit diagram.
2. One of the two transformers primary is tapped at 86.6% and is connected to 3-phase supply.
3. 3-phase supply is fed to the circuit and readings are noted down under no load condition.
4. Loads are connected at secondary side to the two transformers and balanced loads are applied gradually then currents are balanced i.e. $I_1 = I_2$. Readings of V, I, W are noted down.
5. Unbalanced loads are applied, and then the currents I_1 & I_2 are also different. Again the readings of V, I, W are noted down.
6. Efficiencies of balanced and unbalanced loads are found.
7. A graph between efficiency and current I_A are plotted.




G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
 Accredited by NBA of AICTE & NAAC of UGC
 Affiliated to Jawaharlal Nehru Technological University Anantapur,
 Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Observations:

	Voltage(V)	I/P Power(W_1+W_2)		W	I_A	I_B	I_C	V_1	I_1	V_2	I_2	% $\eta = (V_1 I_1 + V_2 I_2) / \text{Input Power (W)}$
		W_1	W_2									
Balanced Loads												
Unbalanced Loads												

Graphs:

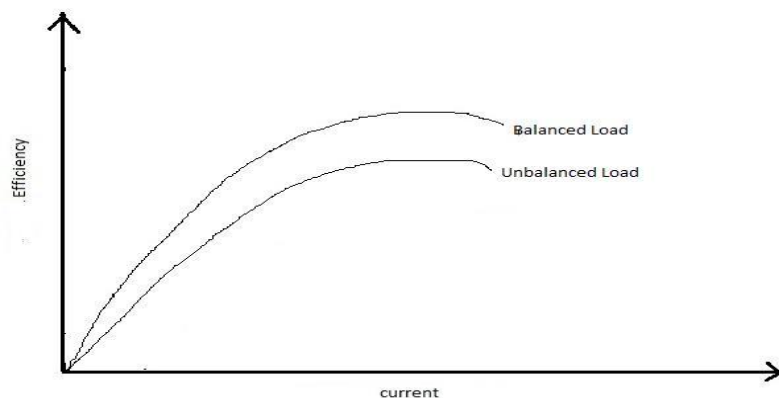



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

SAMPLE CALCULATIONS:

Input Power = $W_1 + W_2 = \text{Watts}$;

Output Power = $V_1 I_1 + V_2 I_2 = \text{Watts}$

Efficiency (η) = $(\text{Out Power} / \text{Input Power}) \times 100$

Result:

Remarks if any:



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Viva Questions:

1. What is phase displacement for 3- ϕ to 2- ϕ system. Give any two applications of scott connection.
2. What is tapping point for Teaser and Main transformer? Teaser and Main transformers must be identical (or) not?
3. What about the position of neutral point in scott connected transformers.
4. What about KVA rating of scott- connected transformers?
5. Derive the conversion of 3- ϕ to 2- ϕ by the vector diagram?



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

SEPARATION OF CORE LOSSES OF A 1- Φ TRANSFORMER

Expt. No:

Date:

Objective:

To separate the iron losses of a single-phase transformer i.e. hysteresis and eddy current losses.

Apparatus:

S.No	Name of the Equipment	Range	Number


Name plate details:

Fuse ratings:



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

CIRCUIT DIAGRAM:

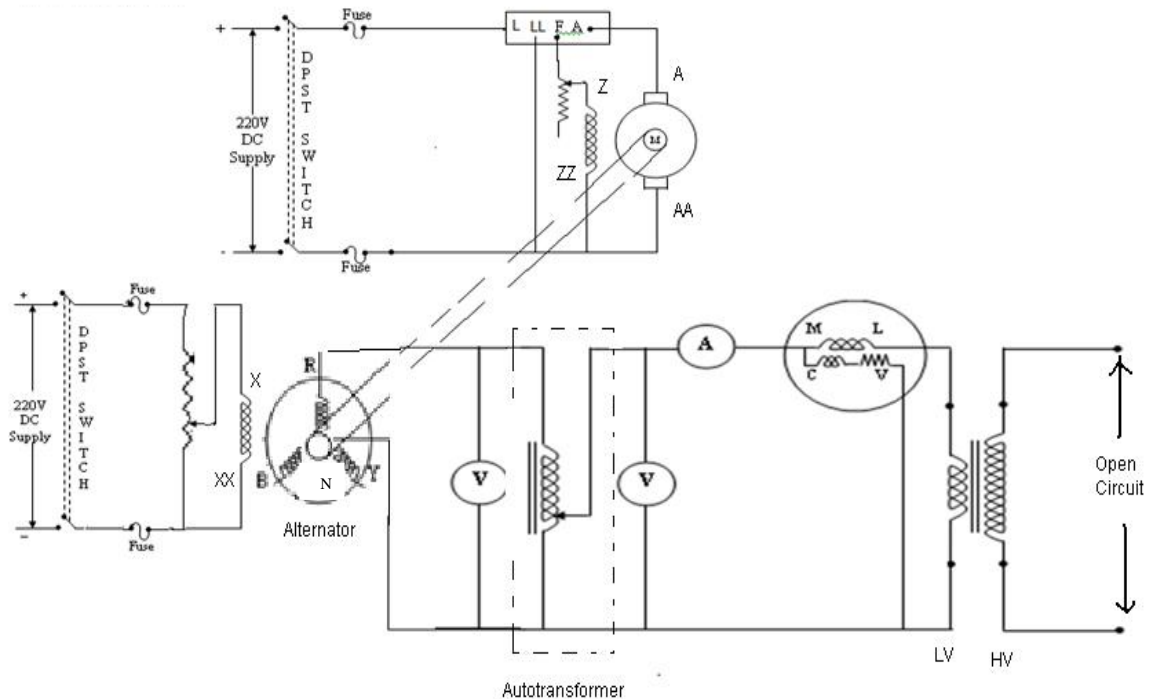

Theory:

There are mainly two types of losses in a transformer. i.e. Core loss (Iron losses) and Ohmic (Copper) losses. Core loss mainly depends on frequency and maximum flux density when the volume and thickness of core laminations are given.

Hysteresis and eddy current losses are called iron losses and takes place in the core of the transformer. i.e. $P_c = P_h + P_e$. Also it is known that $P_h = K_h f B^x m$ and $P_e = K_e f^2 B^2 m$

K_h is proportionality constant that depends upon the volume and quality of the material. K_e is proportionality constant that depends upon the volume, resistivity of the core materials, thickness of the laminations and the units employed.

Eddy current losses also depends on the frequency f is given by $W_e = K B_{max}^2 f^2 t^2 = Bf^2$

Where B_{max} = Maximum flux density in the core weber/m²

f = Frequency (cycles / seconds) in Hz

The iron losses will be expressed by

$$P_c = P_h + P_e = K_h f B^x m + K_e f^2 B^2 \quad m = Af + Bf^2$$

$$P_c/f = A + Bf$$

This is a equation of straight line $y=mx+c$, when $y=P_c/f$, $C=A$

and $m=B$ Eddy current & hysteresis losses can be separated


when A & B are found

The variable frequency supply is obtained from an alternator when frequency can be varied.



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Graphs:

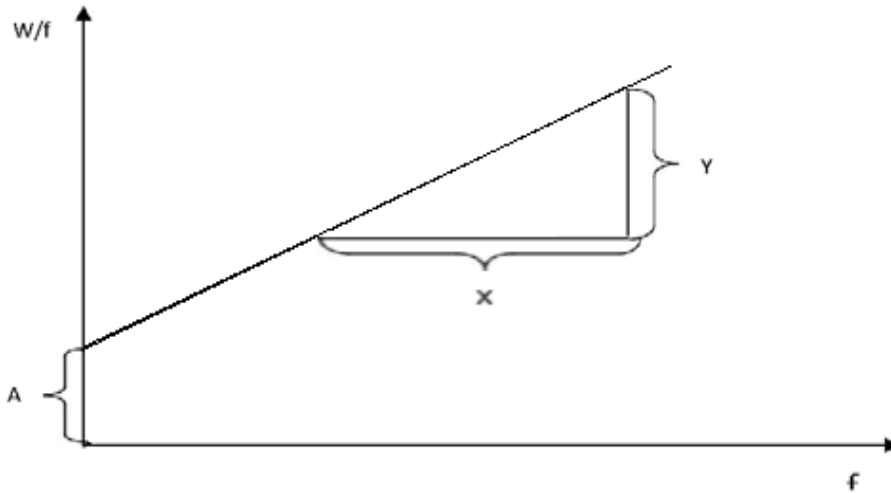

SAMPLE CALCULATIONS:

From the graph

$$K_1 = A = C =$$

$$K_2 = m = B = y/x = \text{slope of the line} =$$

$$\text{Therefore } P_h = Af; P_e = Bf^2$$

For a frequency of 50 Hz then $P_h =$; $P_e =$

Result:

Remarks if any:



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))

Viva Questions:

1. What are the conditions to perform the test separation of losses why?
2. If the thickness of laminations is reduced in a transformer what will be effect on core loss.
3. Transformer designed to operate at 50Hz is operated at rated voltage and 60Hz. How it will change core loss of transformer?
4. What will happen in core loss, if a part of transformer core is replaced by a wood?
5. What are the assumptions made for ideal transformer?



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))



G. PULLA REDDY ENGINEERING COLLEGE (Autonomous): KURNOOL
Accredited by NBA of AICTE & NAAC of UGC
Affiliated to Jawaharlal Nehru Technological University Anantapur,
Ananthapuramu
B.Tech –IV Semester (Scheme-20)
Electrical Machines – I Laboratory (EMC-I (P))